

18. Explain the functions of an 8 : 1 multiplexer.
 19. Draw the logic diagram of a hexadecimal up counter and explain the operation.
 20. Draw the block diagram of a dual slope ADC and explain the conversion process.
-

S.No. 1868

12UEL02

(For the candidates admitted from 2012-2013 onwards)

B.Sc. DEGREE EXAMINATION, NOVEMBER 2017.

Second Semester

Electronics and Communication

APPLIED DIGITAL ELECTRONICS

Time : Three hours

Maximum : 75 marks

SECTION A — (10 × 2 = 20 marks)

Answer ALL questions.

1. Find the decimal equivalent of $(24)_8$.
2. Convert $(95)_{10}$ into Excess-3 code.
3. What is the dual theorem of $A \cdot \bar{A} = 0$?
4. $1101 + 1000 = ?$
5. Draw the logic symbol and truth table of OR gate.
6. What is a full adder?
7. Draw the truth table of a D-flip flop.

8. What is a register?
9. Mention the different types of ADC.
10. Find the resolution of an 8-bit DAC.

SECTION B — (5 × 5 = 25 marks)

Answer ALL questions.

11. (a) Convert the decimal number 127 into following codes.
 - (i) Binary
 - (ii) BCD
 - (iii) Hex.

Or

- (b) Explain Binary to Gray and Gray to Binary conversion.
12. (a) Perform the following Binary operations.
 - (i) $10000 - 01111$
 - (ii) 1010×110
 - (iii) $1100 \div 0011$.

Or

- (b) State and prove demorgan's theorem.

13. (a) Realize the basic logic gates using NOR gate.

Or

- (b) Explain the functions of a 3-to-8 line decoder.
14. (a) Describe the function of an RS flip flop.

Or

- (b) Explain the operation of a 4-bit ring counter.
15. (a) Explain the working principle of a 4-bit weighted resistor DAC.

Or

- (b) Draw the block diagram of a counter ramp ADC and explain the operation.

SECTION C — (3 × 10 = 30 marks)

Answer any THREE questions.

16. Perform the following conversions
 - (a) $(101011101)_2 = \text{—————}_{10}$
 - (b) $(2060)_{10} = \text{—————}_{16}$
 - (c) $(3764)_8 = \text{—————}_2$
 - (d) $(1011\ 0001\ 1001\ 01)_2 = \text{—————}_{16}$.
17. Minimize the following logic function using k-map
 $y = \Sigma m(0, 2, 3, 6, 7) + \Sigma d(8, 10, 11, 15)$.