

PART C — (3 × 10 = 30 marks)

Answer any THREE questions.

16. Explain with suitable example, the colour coding of resistors.
  17. Explain the following terms :
    - (a) 'Opens' in a series circuit and
    - (b) 'Short' in a series circuit.
  18. State super position theorem. Explain it with a suitable example.
  19. With suitable sketches, explain the measurement of period and frequency.
  20. Obtain the expression for frequency of resonance in parallel resonance circuit.
- 

S.No. 2253

17UELS01

(For the candidates admitted from 2017 – 2018 onwards)

B.Sc. DEGREE EXAMINATION, NOVEMBER 2017.

First Semester

Electronics and Communication

SBEC – 1: APPLIED ELECTRIC CIRCUITS

Time : Three hours

Maximum : 75 marks

PART A — (10 × 2 = 20 marks)

Answer ALL the questions.

1. What is power rating of a resistor?
2. Define the term : Inductance.
3. State Kirchoff's voltage law.
4. What do you mean by a voltage division rule?
5. State Thevenin's theorem.
6. State Norton's theorem.

7. Define the terms :
- (a) Peak value and
  - (b) Peak – to – Peak value
8. What is meant by power factor?
9. What is capacitive reactance?
10. State the condition for resonance.

PART B — (5 × 5 = 25 marks)

Answer ALL questions.

11. (a) Derive an expression for energy stored in a capacitor.
- Or
- (b) Discuss the factors governing the inductance of an inductor.
12. (a) State and explain Ohm's law.
- Or
- (b) Explain current division rule with suitable example.

13. (a) State and explain maximum power transfer theorem.

Or

- (b) A radar antenna has a Thevenin voltage of  $100\mu V$  and a Thevenin resistance of  $50\Omega$ . What should be the value of load resistance to obtain the maximum load power? What is the maximum load power?

14. (a) What is average value? Obtain its expression.

Or

- (b) Explain the term : RMS Value.

15. (a) Give a brief account on RL circuit in series.

Or

- (b) A 200 volt 50 cycle source supplies a series RC circuit,  $R=30$  ohms and  $C=79.5\mu f$ . Find
- (i) The impedance
  - (ii) The current
  - (iii) Power factor
  - (iv) Power.